


```

module          crc16_sys;

// Regs/wires/integers
reg            clk, reset_l, crc16_di, crc16_en;
wire [15:0]   crc16_o;
integer       i, mask;
reg [7:0]     crc16_di_8[15:0];

// Simulation target
crc16 crc16(.crc16_di(crc16_di), .crc16_en(crc16_en), .crc16_o(crc16_o),
reset_l(reset_l), .clk(clk));

//-----
// Simulation vector
//-----
initial
begin
    $readmemh("crc16_di.dat", crc16_di_8);

    clk      <= 1'b1;
    reset_l  <= 1'b0;
    crc16_en <= 1'b0;
    crc16_di <= 1'b0;
#110 reset_l <= 1'b1;
#10  crc16_di <= 1'b0;

    for(i = 0; i < 16; i = i + 1)
    begin
        for(mask = 8'h80; mask > 0; mask = (mask >> 1))
        begin
            crc16_di_gen;
        end
    end

#100 $finish;
end

// 20MHz clock generator
always #25  clk <= ~clk;

//-----
// Tasks
//-----
task  crc16_di_gen;
begin
    if(((i % 8) == 1) && (mask == 8))  reset_l <= 1'b0;
    else                               reset_l <= 1'b1;
    if((crc16_di_8[i] & mask) == 0)  #50 crc16_di <= 1'b0;
    else                               #50 crc16_di <= 1'b1;
    if(((i % 8) > 1) && ((i % 8) < 6))  crc16_en <= 1'b1;
    else                               crc16_en <= 1'b0;
end
endtask

endmodule

```

(2) Target module (crc16.v)

Making a simple block diagram is recommended.

```

//-----
// CRC16 (X16+X15+X2+X0)
//  crc16.v
//-----
module crc16(crc16_di, crc16_en, crc16_o, reset_l, clk);

// I/O definition
input      crc16_di;      // CRC16 data          (H)
input      crc16_en;     // CRC16 enable       (H)

```

```

input      reset_l;      // Reset          (L)
input      clk;          // Clock          (X)

output [15:0] crc16_o;    // CRC16 out      (H)

// Regs for random logic
reg        crc16_0_in, crc16_2_in, crc16_15_in;

// Regs for DFFs
reg [15:0] crc16_o;


//-----
// Random logic
//-----
always @(crc16_di or crc16_o or crc16_0_in)
begin
    crc16_0_in <= (crc16_di ^ crc16_o[15]);
    crc16_2_in <= ~(crc16_0_in ^ crc16_o[1]);
    crc16_15_in <= ~(crc16_0_in ^ crc16_o[14]);
end

//-----
// DFFs
//-----
always @(posedge(clk) or negedge(reset_l))
begin
    if(~reset_l)    crc16_o[15:0] <= 1'b0;
    else
    begin
        if(~crc16_en)    crc16_o[15:0] <= crc16_o[15:0];
        else
        begin
            crc16_o[15] <= crc16_15_in;
            crc16_o[14:3] <= crc16_o[13:2];
            crc16_o[2] <= crc16_2_in;
            crc16_o[1] <= crc16_o[0];
            crc16_o[0] <= crc16_0_in;
        end
    end
end

endmodule

```

(b) Verilog simulation result

 

“crc16_di” is an input to the CRC16 generator. This contains USB SYNC code, command code, data, and original CRC16 data to be compared with this CRC16 generator result.

“reset_l” resets the contents of CRC16 registers to prepare CRC calculation.

“crc16_en” is a timing signal to enable CRC16 calculation that applies to data field only.

“crc16_o[15:0]” is a result of CRC16 calculation. After the original CRC16 data is received in full, they are compared to see if they match. CRC error is identified by the mismatch.